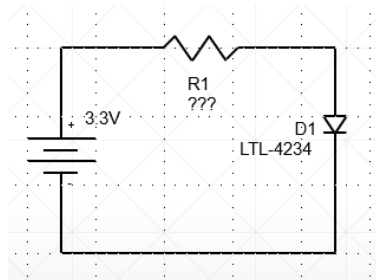


ENGI301: Assignment #1

Due: 09/05/2023 8pm

- 1) **Resistor color codes:** What are the 4-band resistor color codes for the following resistor values (all 5%):
 - a. 22 Ohm
 - b. 330 Ohm
 - c. 1k Ohm
 - d. 2.2k Ohm
 - e. 4.7k Ohm
 - f. 10k Ohm
 - g. 100k Ohm
- 2) **Equivalent resistance:** Show circuit diagram with values for how to create the following resistors with the given approximate value (Use the resistor values from Question 1; There are multiple correct answers for b & c; Answers should have resistance within 1% of specified value):
 - a. 250 Ohm resistor using 2 resistors (Hint: $(R1 \parallel R2)$)
 - b. 2500 Ohm resistor using 3 resistors (Hint: $(R1 + (R2 \parallel R3))$)
 - c. 1750 Ohm resistor using 4 resistors (Hint: $((R1 \parallel R2) + (R3 \parallel R4))$)
- 3) **Resistor Tolerance:** For the 250 Ohm resistor created in Question 2, given that each resistor has a tolerance of 5%, what is the minimum and maximum value of the resistor (rounded to the nearest ohm)?
- 4) **Circuit Analysis:** Using an LTL-4234 LED, what should the resistor value (standard 5%) be for the following circuit such that the LED has maximum brightness (highest forward current) over the entire temperature range.



- 5) **Circuit Analysis:** The circuit below is based around a TL5209. Given that V_{IN} is 5V and $R1 = 280K$ Ohms (1%) and $R2 = 470K$ Ohms (1%). Answer the following questions:
 - a. What is V_{OUT} (to the nearest tenth of a volt)?
 - b. Based on resistor variation alone, what is the maximum and minimum V_{OUT} ?
 - c. What is the output voltage accuracy of the TL5209 over the entire temperature range?
 - d. Given a stable output current of 500mA @ 25C, what is the typical power efficiency (P_{OUT} / P_{IN}) of this regulator? (Hint: Search "LDO power efficiency" on Google)

